

DIGITAL SYSTEMS LABORATORY WORK
MODUL 6 : THE MAP KARNAUGHT



By :

NUR ANNIDA I'FFAH SUPARDI

L200183147

INFORMATION TECHNOLOGY
FACULTY OF COMMUNICATION AND INFORMATICS
UNIVERSITY OF MUHAMMADIYAH SURAKARTA

NIM : L200183147
 Name : Nur Annida I'ffah Supardi
 Assistant Name : Salsa Sasmita Mukti
 Date of Practicum : Friday, April 26 st 2019


Attempt 1

1. Create a combination of logic gates based on the following map.

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	1	1	1	0
	11	0	1	1	1
	10	0	0	0	0

2. Boolean function : $F = A'C'D + BD + ACD$

3. Create logic gates based on your boolean function! Picture in the box below!

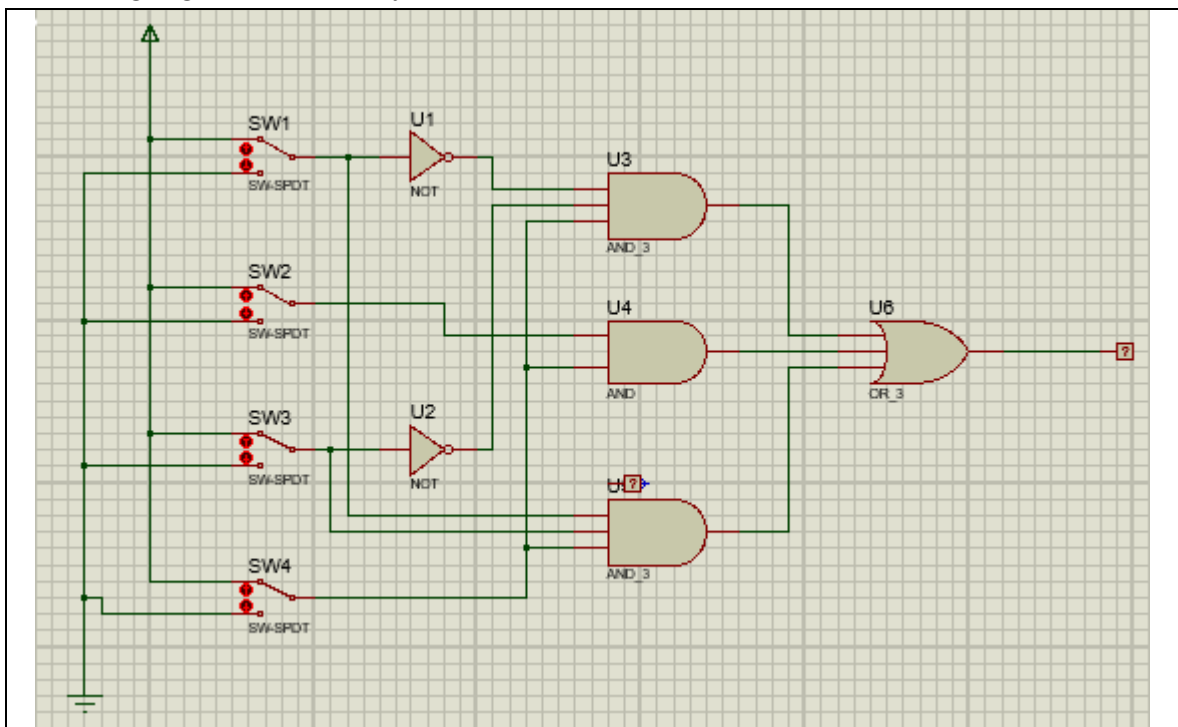

Attempt 2

1. Create a combination of logic gates based on the following map.

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	0	0	1


2. Boolean function :

$$F = B'D' + BD \quad (\text{AND-OR})$$


$$F = (B'+D)(B+D') \quad (\text{OR-AND})$$

3. Create logic gates based on your boolean function! Picture in the box below!

SOP

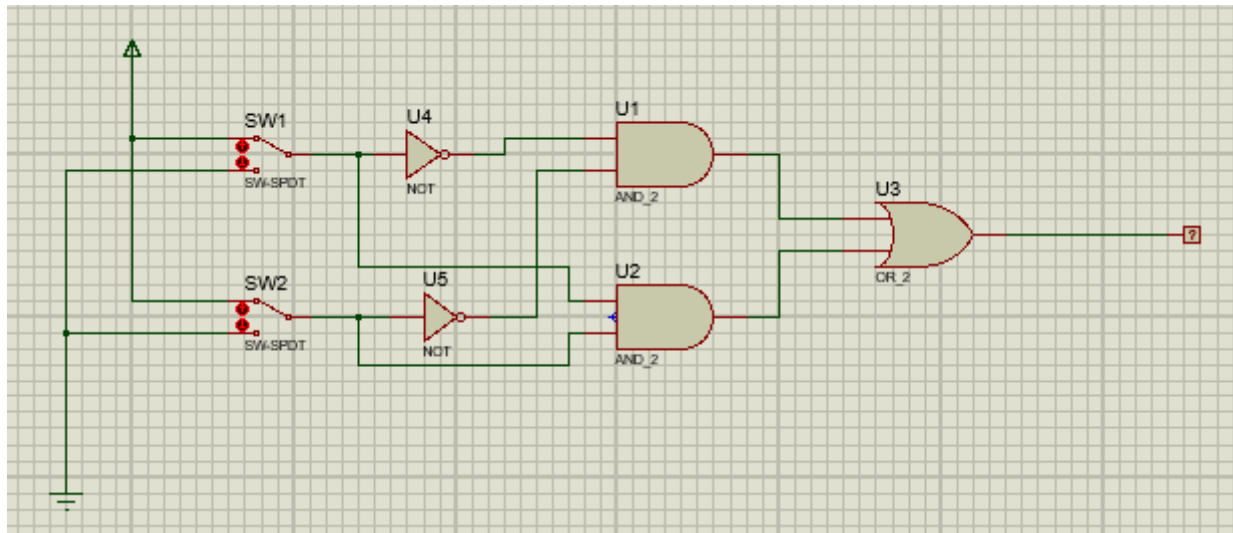

POS

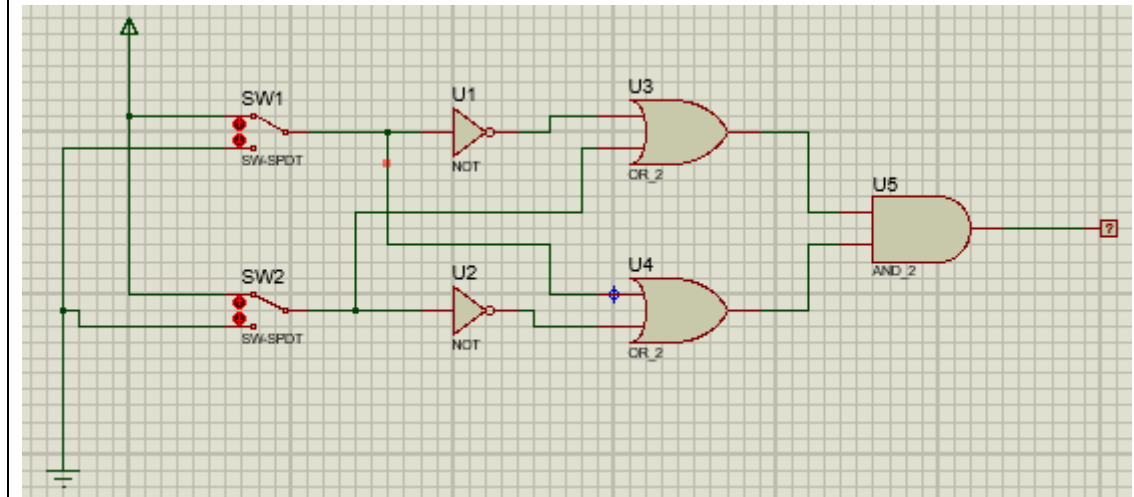

Do the two combinations give the same results? Yes or No


- $F = BD + B'D'$
- $F = (B'+D)(B+D')$
 $= B'B + B'D' + BD + DD'$
 $= 0 + B'D' + BD + 0$
 $= B'D' + BD$
 $= BD + B'D'$

Attempt 3

1. Boolean function : $F = XYZ + XYZ' + XY'Z + X'YZ + X'YZ' + XY'Z' + X'Y'Z'$.
2. Based on the boolean function, fill in the points on the map karnaugh of the following!

		XY			
		00	01	11	10
Z	0	1	1	1	1
	1	0	1	1	1

3. Simplify boolean functions : $F = X + Y + Z'$
4. Create logic gates based on your boolean function! Picture in the box below!

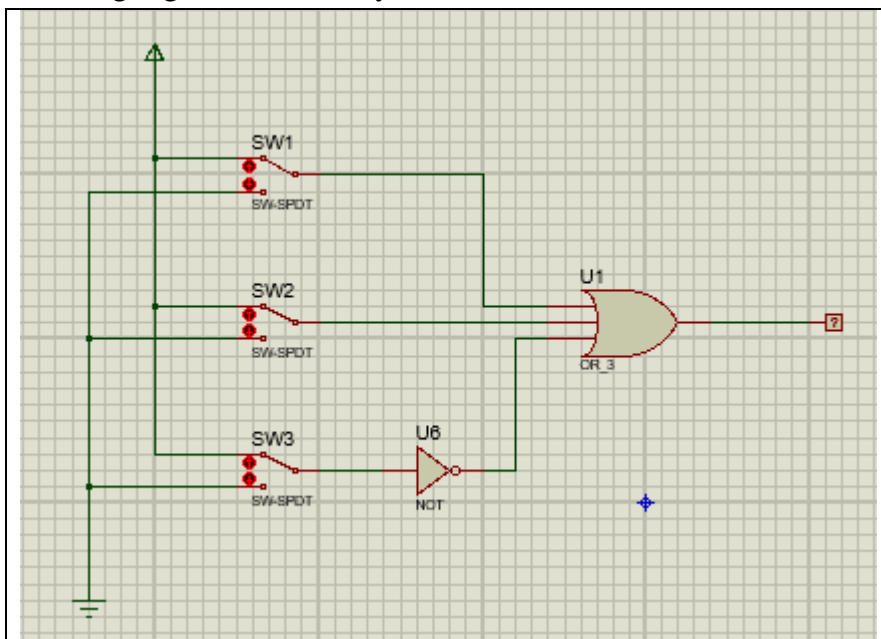


Attempt 4

1. Boolean function : $F = AD' + ABC + ABC' + BCD + BC'D + AB'CD'$.
2. Based on the boolean function, fill in the points on the map karnaugh of the following!

		AB			
		00	01	11	10
CD	00	0	1	1	1
	01	0	0	1	0
	11	0	1	1	0
	10	0	0	1	1

3. Simplify boolean functions : $F = BC'D' + AD' + AB + BCD$

4. Create logic gates based on your boolean function! Picture in the box below!

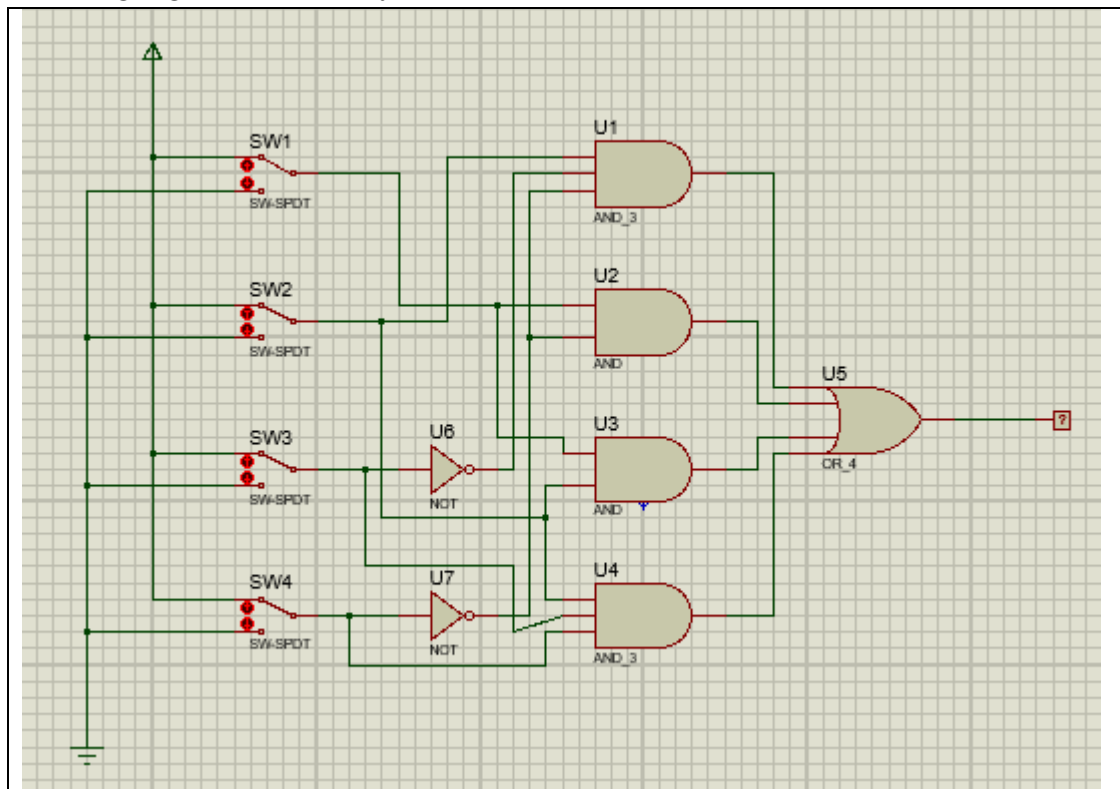

Attempt 5

1. Table of boolean function:

A	B	C	D	F
0	0	0	0	1
1	0	0	0	0
0	1	0	0	0
1	1	0	0	1
0	0	1	0	1

1	0	1	0	1
0	1	1	0	0
1	1	1	0	0
0	0	0	1	1
1	0	0	1	1
0	1	0	1	0
1	1	0	1	1
0	0	1	1	1
1	0	1	1	0
0	1	1	1	1
1	1	1	1	0

2. Based on the table. Fill in the points on the map karnaugh of the following!

		AB			
		00	01	11	10
CD	00	1	0	1	0
	01	1	0	1	1
	11	1	1	0	0
	10	1	0	0	1

3. Simplify boolean functions :

$$\mathbf{F = A'B' + A'CD + ABC' + AC'D + B'CD'}$$

4. Create logic gates based on your boolean function! Picture in the box below!

